

Modifications to the Motorola UHF Micor mobile transceiver for use with high speed FSK Data Modems

It is assumed that those attempting this conversion will have the test equipment, service manuals, and expertise necessary to tune and service this radio.

THIS IS DEFINITELY NOT THE RADIO FOR BEGINNERS.

Please review the conversion instructions before you begin. In several areas, there are two sets of instructions, one set is for use with a TAPR/G3RUH modem, the other is for use with a TPRS Texnet modem. You might want to mark the steps that apply to your modem. This could prevent some confusion and possible mistakes during the conversion process.

The UHF Micor mobile radio is a fine high power UHF radio. This unit is a true "cadillac" radio that incorporates many advanced features.



The transmitter employs a heterodyne exciter. Receiver oscillator injection is mixed with the signal from an offset oscillator to generate the transmit frequency. The offset oscillator is varactor modulated for true FM.

The receive channel element output is multiplied by 24 and serves as the main frequency determining element for both the

receiver and the transmitter. Since one oscillator serves both the receiver and transmitter, the transmit frequency will "track" the receive frequency as it changes with temperature.

The transmitter incorporates a circulator in the antenna output network to protect the PA transistors from high SWR. The presence of a circulator insures that the UHF Micor will be a "good neighbor" when installed at a site that is shared by other services.

Before proceeding any further, take a few minutes to become familiar with the radio that you plan to convert. Refer to the illustrations in the Motorola Service Manual for the location of major components.

Now that you know the physical layout of the radio, let's cover some of the technical aspects.

What is the transmit power output ?

The answer to this question can be found by looking at the model number. The chart below translates these numbers into useful information.

While the model number may contain a combination of 11 or more numbers and letters, the first 5 of these are the ones of interest. The rest describe various options such as " PL ".

<u>Model</u>		<u>Transmit current</u>
T34RTA	25W	10.5 A @ 13.6 V
T44RTA	45W	15.9 A @ 13.6 V
T54RTA	75W	25.0 A @ 13.4 V
T74RTA	100W	35.5 A @ 13.4 V

As you can see, the 75 and 100 watt radios draw a lot of current on transmit. If you have one of these radios and you don't need that

much RF or your power supply can't handle the load, don't worry. There is a power adjust control that will allow you to lower the power. For the record, I would not recommend reducing the TX power more than 50 % with this control. Any greater reduction might lead to instability in the PA stages.

Before ordering crystals and conversion parts you must determine the exciter configuration for your radio. The following information covers the most common configurations.

A standard exciter UHF Micor transmits 5 MHz higher than it receives.

A wide-spaced exciter has 2 offset oscillators. One provides +5 MHz transmit. The other is for simplex operation or talk-around as it's known in the commercial two-way field.

The 11.7 MHz exciter is configured for simplex operation.

The most common exciter is the standard +5 MHz version. With one exception, you will need to remove the exciter board in order to determine which version is installed in your radio. The *one* exception is the wide-spaced exciter. Before removing the exciter board, check for the presence of a second exciter output network *L402-L407*. If you have this network, you have a wide-spaced exciter.

If you don't have the network, proceed with removal of the exciter board. Locate the offset oscillator crystal. It should be the only crystal on the board. If it's marked 16700, then you have a standard exciter. This version requires that you change the 16.7 MHz crystal to 11.7 and make several component changes. If you have an 11700 crystal, you have a simplex exciter.

Simplex and wide-spaced exciters require no crystal or component changes. The only change necessary is conversion from voice to FSK data modulation.

If your crystal is marked 14700, STOP! You have a 470-512 MHz radio and conversion isn't practical if not impossible.

This would be a good time to check the parts list in Appendix C and order the crystals and conversion parts.

The major problem in conversion happens when you decide to add a preamp to the receiver. Some preamps will not work with this radio. The antenna network is picky about the load impedance presented to the receiver port. The WA5VJB preamps commonly used with the RCA 700's act like an attenuator when used in a Micor. Several preamps that will work are the Ramsey PR-40, and the original equipment Motorola TLE-8192A. Physical size and price make the PR-40 the best choice. Unless you can find a TLE-8192A on the surplus market, skip this one. Current price on a new 8192A is \$171.00.


Important note: If possible, check the radio at its original operating frequency before you proceed with conversion.

With the basics covered, it's time to begin conversion.


PL Encoder and decoder removal.

If you do not have an encoder or decoder, skip to step 3. If you have one board but not the other, follow step 1 or 2 and then skip to 3.

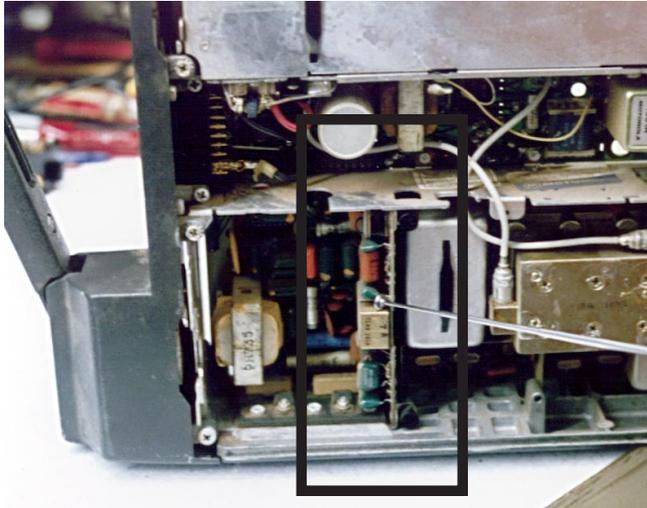
1. Remove RX PL decoder board (if installed). This board plugs in to the audio-squelch board from the bottom side of the radio. The decoder location is shown in the bottom view of the radio.



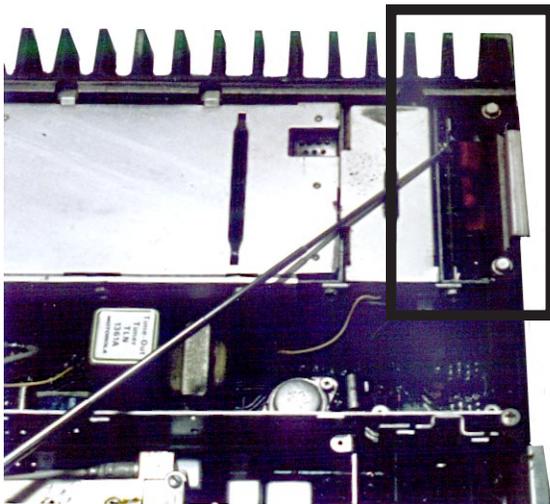
2. Remove the TX PL encoder (if installed). This board plugs into the exciter board from the bottom side of the radio. The encoder board location is also shown in the bottom view of the radio.



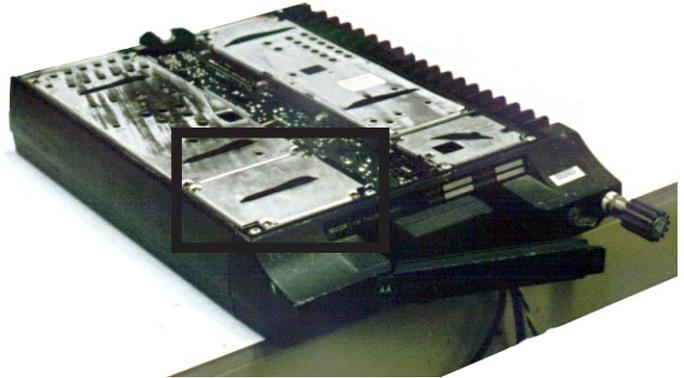
3. Remove the audio-squelch board. This board is held in place by 4 screws and is removed from the top side of the radio.



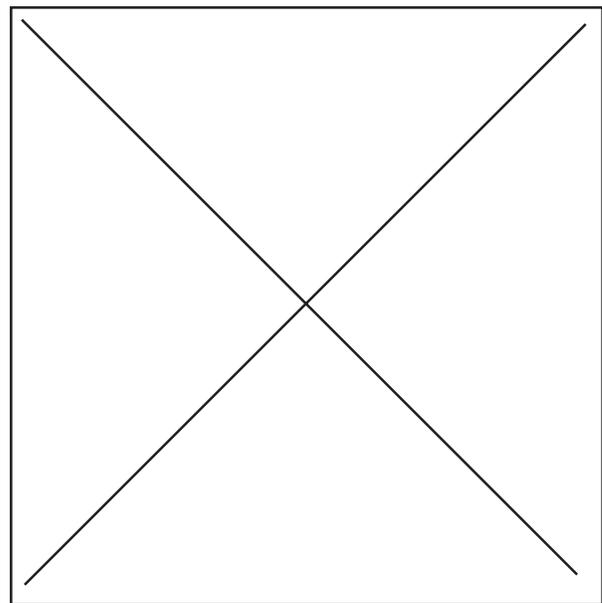
Refer to the audio squelch board layout for the location of JU201. If JU201 is not installed, add this jumper using a short length of insulated wire. This finishes work with the audio squelch board. When you place this board back in the radio, be sure that the 6 pins that plug into the audio power amplifier board (2 transistors on a heatsink mounted to the side of the radio) mate correctly.



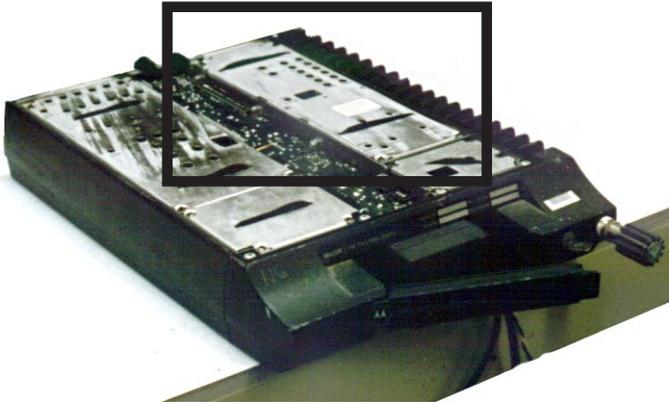- Remove the exciter board. This board is held in place by 7 screws. You will also need to remove 2 (or 3 WS) phono plug connections. One is the exciter output connection to L302-307 (also a connector to L402-L407 WS), the other is the injection from the receiver to the exciter. This connection is made on the component side of the board.




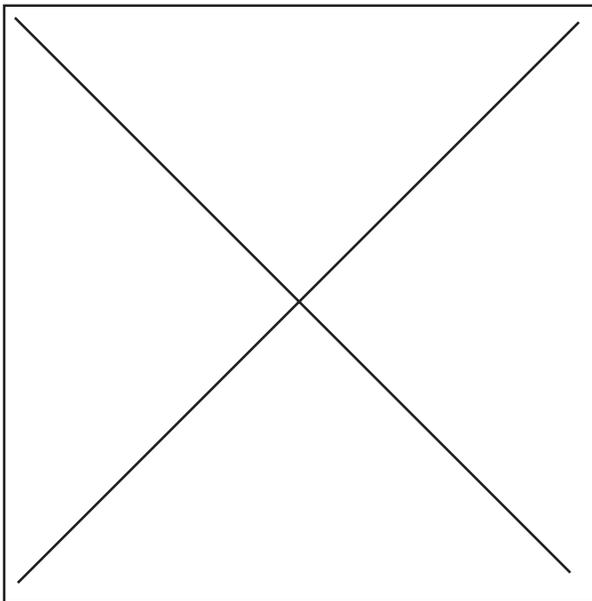- Refer to the exciter layout showing the location of P401. Add a jumper (if one is not present) between P401-2 and P401-4. Note that the circuit traces that connect to pins 2 and 4 extend to pads on the left side of P401. Install an insulated jumper at this location.




Receiver modifications.

- Disable RX AFC. There is an alignment access hole at the left rear of the RX shield cover with the label "AFC OFF". Insert a felt tip marker into the hole and mark the circuit pad on the receiver board that corresponds to this test point. Remove the shield cover and install a jumper wire from this pad to ground. For those working from schematics, this is the same as soldering a jumper across C115.

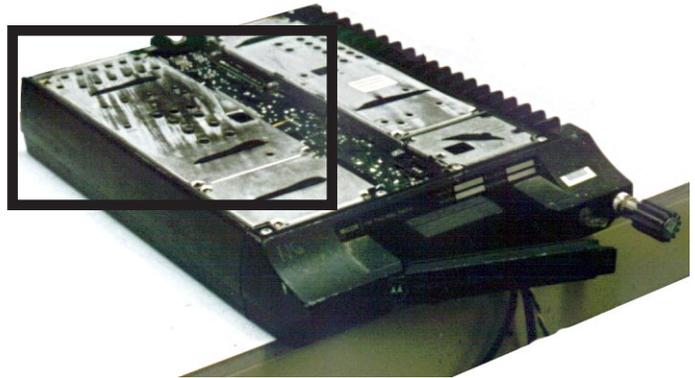

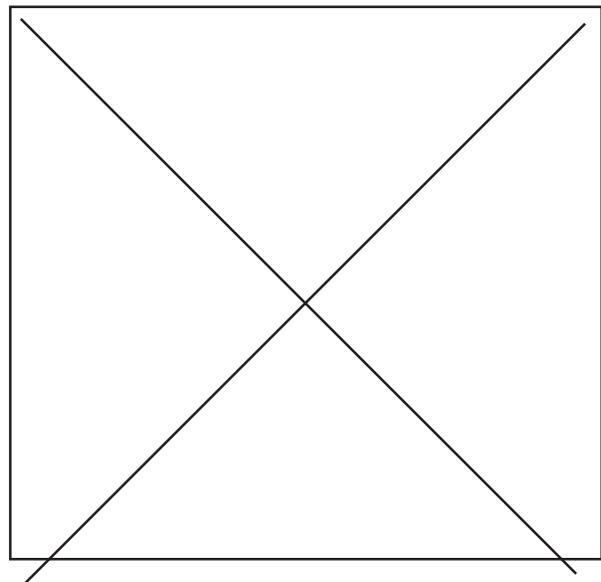- Select the F1 channel element position. Solder a jumper wire between pins 1 and 2 of P904. P904 is the group of connector pins that connect the receiver RF IF board to the control interconnect board. P904 is divided into 2 parts. Pins 1-9 are toward the rear of the radio and pins 10-16 are near the front.




If you are using a TAPR/G3RUH Modem, skip steps 3 ,4, 10 and 11.

3. Refer to Appendix A for the data inverter schematic. Build the data inverter on a small piece of perfboard. You may choose to install the volume and squelch pots on this same piece of board. *The volume and squelch pots are optional. They are not needed for data. You can omit them unless you want to use a speaker to monitor channel activity.*

Before you decide to skip installation of the volume and squelch pots, be advised that you will need to make temporary provisions for these controls during receiver alignment

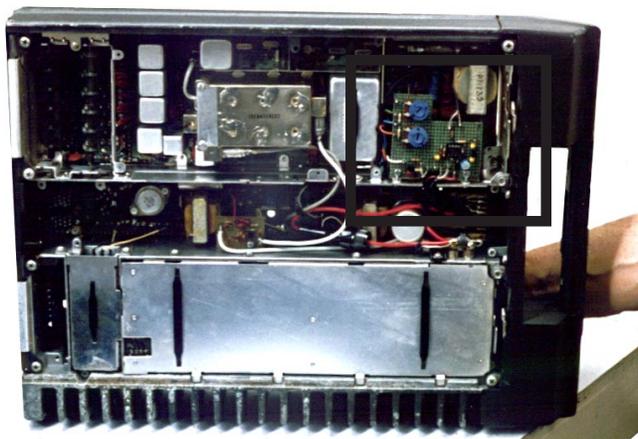4. After you have completed the data inverter, use small "L" brackets to mount the board to the shield that separates the control interconnect board and the receiver circuits. The preferred mounting position is on the receiver side of the shield and located over audio squelch board.




Picture of Perf Board for TPRS Modem modification. Mounted in Upper Right Corner.

If you are using a TAPR/G3RUH modem, follow steps 5a and 6a. If you are using a TPRS modem, follow steps 5b and 6b.

- 5a. Cut the leads of a 10K and a 15K 1/4 w resistor to 1/4 ". Solder one lead of the 10K resistor to pin 15 of J904. J904 is the connector on the control interconnect board that mates with P904 on the receiver RF-IF board. Exercise caution when soldering the resistor lead. Do not inadvertently solder the connector pin on the RF-IF board to the receptacle pin on the interconnect board. Solder a 15K resistor from the "free" lead of the 10K resistor to ground.

- 5b. Cut the leads of a 150K 1/4 w resistor to 1/4 ". Solder one lead of this resistor to pin 15 of J904. J904 is the connector on the control interconnect board that mates with P904 on the receiver RF-IF board. Exercise caution when soldering the resistor lead. Do not inadvertently solder the connector pin on the RF-IF board to the receptacle pin on the interconnect board.

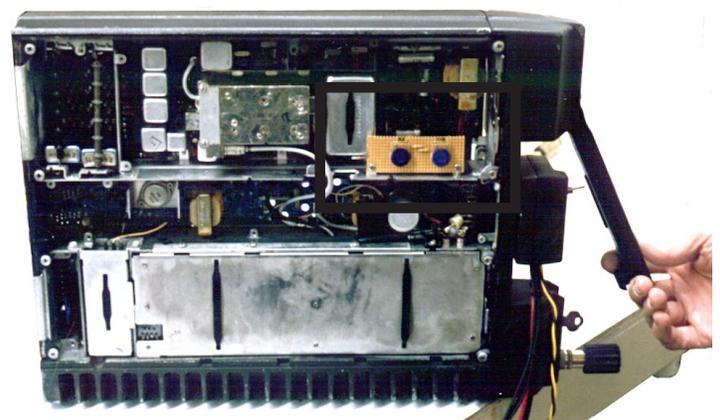- 6a. Prepare a 7 " length of RG-174 or similar shielded cable. Connect the center conductor to the junction of the 10K and 15K resistors. Solder the shield to the ground foil on the interconnect board.



Picture of Perf Board for TAPR/G3RUH Modem modification. Mounted in Upper Right Corner.

Pin 16 of P904 is connected to ground and the foil that connects to this pin is a good place for the shield connection. It may be necessary to use a screwdriver or Xacto knife to remove some of the protective coating that covers the ground foil. The free end of this coax will be connected to the power plug in step 1a under the heading *Data Connections*.

- 6b. Prepare a 10" length of RG-174 or similar shielded cable. Connect the center conductor to the free end of the 150K resistor. Solder the shield to the ground foil on the interconnect board. Pin 16 of P904 is connected to ground and the foil that connects to this pin is a good place for the shield connection. It may be necessary to use a screwdriver or Xacto knife to remove some of the protective coating that covers the ground foil. The free end of this coax will be connected to the data inverter board.

Refer to the Control Interconnect board illustration for the following steps.

7. Solder an insulated jumper wire across pins 5 and 6 of **K902**. This connection can be made on the top side of the circuit board.
8. Solder a 1N4001 or similar diode across pins 1 and 2 of **K901**. The banded end should connect to pin 1.
9. *If you wish to mount the volume and squelch controls in the radio perform the following steps.*


Solder wires to the following pins on the J903. J903 mates with pins on P903 on the audio/squelch board. When soldering to the pins of J903, use caution to keep from soldering the pins on the audio/squelch board to the mating pins on J903. As a precaution you may choose to remove the audio/squelch board.

- Pin 3. The emitter follower output (also known as audio/squelch high).
- Pin 5. Volume arm.
- Pin 6. Chassis ground.
- Pin 9. Squelch.

Refer to the audio/squelch control schematic in Appendix A. If you did not mount the controls and their associated resistors on the data inverter board, devise your own mounting for these components.

Connect the wires from J903 to the appropriate points.

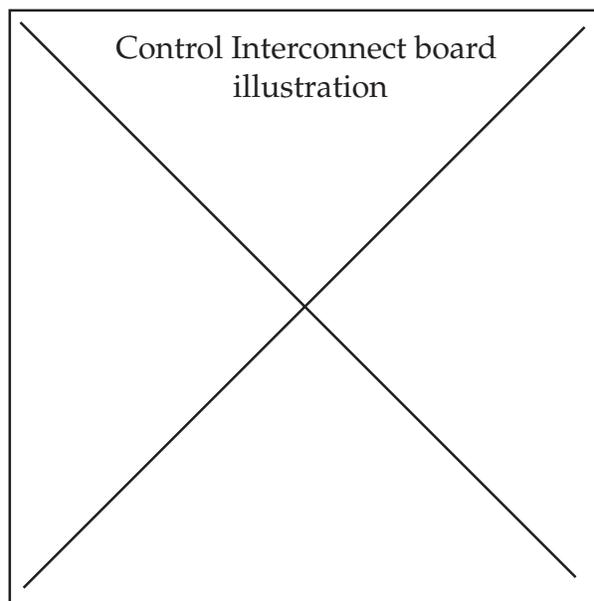10. Power for the data inverter can be obtained at the Extra Filtered A+ point on the control interconnect board. The chassis ground connection can be made on the ground foil adjacent to pin 16 of J904.
11. Connect the shielded cable from the discriminator to the input of the data inverter.
12. If you plan to install a receive preamp, do so at this time. The power connection should be made at the Extra Filtered A+ point.



Data Connections.


Data connections to the outside world are brought out on unused pins on the power plug P901. These connections are as follows:

<u>Pin</u>	<u>Function</u>
27	RX Data
28	RXD shield
29	PTT
30	PTT shield
31	TX Data
32	TXD shield

On some radios (12 frequency) there may be wires connected to these pins. Remove these wires as they are not needed. Follow the wires back to the 12 frequency adapter on the receiver RF board and cut them loose at this point.

If you are using a TAPR/G3RUH modem, follow steps 1a, 2 and 3-7. Don't take a short cut by skipping construction of the buffer amplifier (see appendix ?? schematic). This stage is necessary for proper modem to radio interface. Without it, the radio will exhibit poor frequency stability and the modulation symmetry will be miserable (you may have a deviation of positive 3.5 khz and a negative 2.0 kHz). Follow the exciter modifications . **DO NOT TRY TO USE ANY OF THE EXISTING AUDIO CIRCUITS IN THE TRANSMITTER.**

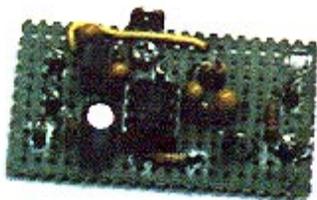If your are using a TPRS modem, follow steps 1b, 2 and 8.



Picture of Perf Board for TAPR/G3RUH Buffer Amplifier.
Schematic in Appendix ??

- 1a. RX Data Out. Connect the shielded cable from the 10K resistor at the RX discriminator output to P901-27 center, P901-28 shield.
- 1b. RX Data Out. Connect a shielded cable from P901-27 center, P901-28 shield, to the RX data inverter output.
2. PTT. Connect a 12 " length of shielded cable to P901-29 center, P901-30 shield. The other end of this cable will be connected in the PTT configuration instructions.
3. TX Data In. Connect a shielded cable to P901 -31 center, P901-32 shield.
4. Build the TX audio buffer /amplifier stage on a small piece of perfboard. Follow the schematic in appendix B. After you have completed the amplifier, use small "L" brackets to mount the board to the shield that separates the control interconnect board and the receiver circuits. The preferred mounting position is on the receiver side of the shield and located over the audio /squelch board.
5. Power for the buffer amplifier can be obtained at the Extra Filtered A+ point on the control inteconnect board. The chassis ground connection can be made on the ground foil adjacent to pin 16 of J904.
6. Connect the shielded cable from P901-31, 32 to the input of the buffer amplifier.
7. Run a piece of shielded cable from the output of the buffer amplifier to the exciter. Route this cable through the hole in the side of the exciter shield compartment. This is the same hole that the receiver oscillator injection cable runs through. Leave 6 to 8 inches of extra cable in the exciter compartment so that the exciter board can be removed with the data cable connected.

8. TX Data In. (TPRS Modem) Connect a shielded cable to P901-31 center, P901- 32 shield. Route this cable from the power plug to a hole in the side of the exciter shield compartment. This is the same hole that the receiver oscillator injection cable runs through. Leave 6 to 8 inches of extra cable in the exciter compartment so that the exciter board can be removed with the data cable connected.

PTT Configuration.

The PTT can be configured in two ways. The first is an active low PTT which is standard on the Micor. The second is an active high PTT. The RCA 700 radios used this polarity. I prefer the active high PTT to maintain compatibility with modems configured for the RCA 700. Select the one that is most appropriate for your application.

If you are using a TAPR/G3RUH modem, follow the instructions for active low PTT.

If the active low PTT output is selected on the TPRS modem, connect the PTT cable from the power plug to the following pins on J910 (the metering control socket on the control interconnect board. Center conductor to pin 5 (PTT) and the shield to pin 6 (Chassis Ground).

If the active high PTT output is selected, build the 2N2222 PTT inverter stage as shown in Appendix A. The PTT cable from the power plug should be connected to the input of this stage and the output should connect to pins 5 (PTT) and 6 (Chassis Ground) of J910.

Exciter Modifications

Two sets of instructions are provided for the exciter modifications. The first set is for the standard +5 MHz exciter. The other set is for those with a wide-spaced exciter.

If you have a 11.7 MHz exciter, follow the +5 MHz conversion and skip all of the component changes in step 6.

+5 MHz Exciter Modifications

Refer to the standard exciter illustration when performing the following steps.

1. Remove the exciter board from the radio.
2. Remove C316 (.001). Install a jumper wire in place of C316.
3. Unsolder the lead of R319 (15K) that IS NOT connected to the same circuit pad as the cathode of varicap diode CR301. Leave this end of R319 free. It will be used later.
4. Install a 100k resistor across the varicap CR301.
5. Locate the trace that runs from the anode of CR301 to the audio section on the other end of the exciter board. This trace is on the component side of the board. Cut this trace adjacent to the connection at CR301
6. Change the following components on the exciter board.

<u>Part #</u>	<u>Old</u>	<u>New</u>	<u>Motorola Part #</u>
C332	36 pf	51 pf	21-82610C07
C333	75 pf	110 pf	21-82610C69
C334	68 pf	100 pf	21-82610C44
L300	Blue	Red	24-83879G10
L310	1.1 uH	1.7 uH	24-82835G12
L311	4.6 uH	6.7 uH	24-82835G29
L312	2.3 uH	3.5 uH	24-82835G11
L313	.57 uH	.82 uH	24-82835G13
R321	15 K	5.6 K	None
Y301	16.7 MHz	11.7 MHz	ICMPrt#167561

7. Connect the shield of the TX data cable to the jumper installed in place of C316.

8. Connect the center conductor of the TX data cable to the free end of R319 (15K). This completes the standard exciter modifications. Re-install the exciter in the radio. Be sure to re-connect the receiver oscillator injection and exciter output cables.

This completes the standard exciter modifications. Re-install the exciter in the radio. Be sure to re-connect the receiver oscillator injection and exciter output cables.

Wide-spaced Exciter Modifications

Refer to the wide-spaced exciter illustration when performing the following steps.

1. Remove the exciter board from the radio.
2. Remove C317 (.001). Install a jumper wire in place of C317.
3. Unsolder the lead of R403 (15K) that IS NOT connected to the same circuit trace as the cathode of varicap diode CR401. Leave this end of R403 free. It will be used later.
4. Install a 100K resistor across the varicap CR401.
5. Cut the circuit board trace that connects one end of R320 to the anode end of CR401.
6. Connect the shield of the TX data cable to the jumper installed in place of C317.
7. Connect the center conductor of the TX data cable to the free end of R403 (15K).

This completes the wide-spaced exciter modifications. Re-install the exciter in the radio. Be sure to re-connect the receiver oscillator injection and exciter output cables.

Radio Alignment

The location of the various alignment points should be clearly marked on the shield covers of the receiver, exciter, and power control boards. Use a VOM on the 50 uA scale when metering the various test points. The various metering points can be determined by the following method.

Look at the meter plugs from the top of the radio. The plug consists of seven pins in two rows. The top row has four pins. The bottom row has three. The top row is read from left to right and the bottom row from right to left. One lead of the VOM will connect to the appropriate metering point and the other lead will connect to ground.

1 2 3 4
7 6 5

As you tune the various stages, it may be necessary to swap the polarity of the meter leads in order to obtain an upscale reading on the VOM.

Receiver Alignment

1. Adjust L101 through L105 to the end of the coil form away from the circuit board.
2. Adjust tuning screws of L106 through L108 until each screw extends about 1/8 "below the receiver shield. Preset tuning screws of L111 through L116 so that the screw end is in the space between the board and its shield, and about 1/8 " from the shield.
3. Meter position 1. Alternately tune L101 and L102 CCW two turns at a time for a peak on Meter 1.
4. Meter position 2. Tune L103 CCW for a peak on M2. Tune L104 CCW for a dip on M2.

5. Meter position 3. Tune L105 CCW for a peak on M3. Tune L104 for a peak on M3. Re-peak both coils.
6. Meter position 3. Detune L101 until meter 3 drops to 10 μ A. Tune L103 for peak M3 reading. Keep this peak below 12 μ A by further detuning of L101 if necessary.
7. Meter position 1. Alternately tune L101 and L102 for peak M1 reading.
8. Meter position 3. Tune L106 for a dip on M3. Tune L107 for a peak on M3. Tune L108 for a dip on M3. Do not repeat.
9. Meter positions 4,5. Discriminator- Inject an 11.7 MHz signal into L110 hole on the receiver shield. Insert the injection probe wire far enough into L110 to obtain a saturated reading on M5. Tune L109 for an exact zero reading on M4. This adjustment is critical.
10. Unsquench the receiver. Connect a signal generator to the antenna connector and set the RF output of the generator to maximum.
11. Using a frequency counter, count the RX injection frequency at the injection output to the exciter. The correct reading will be 11.7 MHz below the operating frequency. Adjust the channel element warp capacitor until the correct reading is obtained.
12. Meter position 4. Adjust the signal generator frequency for an exact zero reading on M4.
13. Meter position 5. Tune L111 through L116 for peak reading on M5. Reduce signal generator output to keep M5 out of saturation. Tune L110 for peak on M5. Repeat adjustment of L111 through L116.
14. Connect a AC voltmeter across the speaker leads. Tune L106 through L108 for best noise quieting (minimum meter reading).

Tune L111 through L116 for best noise quieting. Repeat until no further improvement can be made.

15. If you have installed a preamp, follow the instructions supplied with the preamp and tune for minimum reading on the AC voltmeter. Sensitivity with a preamp will be approximately .25 μ V for 20 dB of quieting or .175 μ V for 12 dB SINAD.

Exciter Alignment

Note: Adjustments that pertain to wide-spaced exciters are enclosed in brackets. If you are converting a wide-spaced radio, skip the adjustments that *are not* enclosed in brackets.

1. Adjust the slug in L301 [L401] so that the end is flush with the circuit board. Adjust the tuning screws in L302 to L307 [L402 to L407] fully CCW until each screw is fully extended. There is a stop on each screw which will keep it from being completely removed from the filter.
2. Meter position 4. Disable offset oscillator. Short TP301 to ground. M4 should read zero when this point is shorted to ground.
3. Connect a wattmeter terminated with a 50 ohm dummy load to the antenna connector.
4. Meter position 2 [3]. Remove the exciter input cable from the receiver RF deck. Connect this cable to a signal generator using the appropriate adapters. Set the signal generator to the desired transmit frequency and set the output level to 50-70 millivolts. Key TX and adjust L301 CW [L401] for a peak reading on M2 [M3]. Adjust the generator output for a M2 [M3] reading at the center of the meter scale.
5. Meter position 2 [3]. With TX keyed, adjust L302 [L402] for minimum M2 [M3] reading. Adjust L303 [L403] for a peak reading. Adjust L304 [L404] for a minimum reading.

Adjust L305 [L405] for a peak reading.
Adjust L306 [L406] for a minimum reading.
Adjust L307 [L407] for a peak reading.
Adjust L302 through L307 [L402 through L407] CW (in) one-half turn each.

6. At this point unkey the transmitter. Continue to supply an on frequency signal to the exciter with the signal generator. Key the transmitter. You should see an indication on the wattmeter. Using the power adjust control, set the output power to the correct level for your radio. If you wish to reduce the output power, **DO NOT** turn the level to less than 20 watts. There is protection circuit that will disable the PA stages if the output power drops too low.
7. Remove the short at TP301. Set the slug in coil L300 [L400] to the center of its range.
8. Disconnect the signal generator and reconnect the exciter input cable to the receiver RF deck.
9. Key the transmitter. You should see RF output. If necessary, use the power adjust control to reset the power to the desired level. If you are using a TPRS modem, the frequency may be 10 or so kHz off until you connect the 9600 baud modem.

If you are using a TAPR/G3RUH modem, follow steps 10 thru 13 to set transmitter frequency and deviation. If you are using a TPRS modem, follow steps 14 thru 18.

10. Connect the radio to the 9600 baud modem.
11. Key the transmitter and adjust L300 [L400] to set the transmit frequency.
12. Using the transmit level pot in the modem, set the deviation to 3 kHz.
13. Re-check transmit frequency setting.

14. Connect the radio to the TPRS 9600 baud modem. Remove output jumper S1 on the modem.
15. Key the transmitter with the modem PTT and adjust L300 [L400] to set the transmit frequency.
16. Install jumper S1 in the modem. Key the transmitter with the modem PTT and set the deviation to 3.0 kHz.
17. Remove jumper S1 and check the transmit frequency. If necessary, adjust L300 [L400] to bring the radio back on frequency.
18. Install jumper S1 and verify that the deviation is still in the area of 3 kHz. The frequency and deviation adjustments tend to interact. If necessary, repeat steps 17 and 18. **DO NOT adjust the transmit frequency without removing jumper S1 in the modem.**

The presence of TX data on the modulator will give a false reading.

Modem Interface Notes

TAPR 9600 baud Modem Modifications

Install a 1 uf monolythic capacitor across C8 in older units, C7 in later versions, a .1 uf monolythic in the RX input circuit.

TPRS 9600 Baud Modem modifications:

1. Remove R28, a 220K resistor.
2. Solder a jumper wire across R29, a 330K resistor.

Both of these resistors are in the RX Data input circuit that feeds pin 3 of IC U10 in the modem. For more information, refer to the modem schematic.

