

The End-Fed Half Wave Antenna

Rogue Valley Amateur Radio Club

Tom McDermott, N5EG


October 6, 2016

Outline

- The End fed antenna is very convenient.
- Where did all that RFI come from?
- How come I'm getting RF bites from my equipment?
- Kirchhoff's current law.
- Antennas obey the law (not your opinion).

Diagram

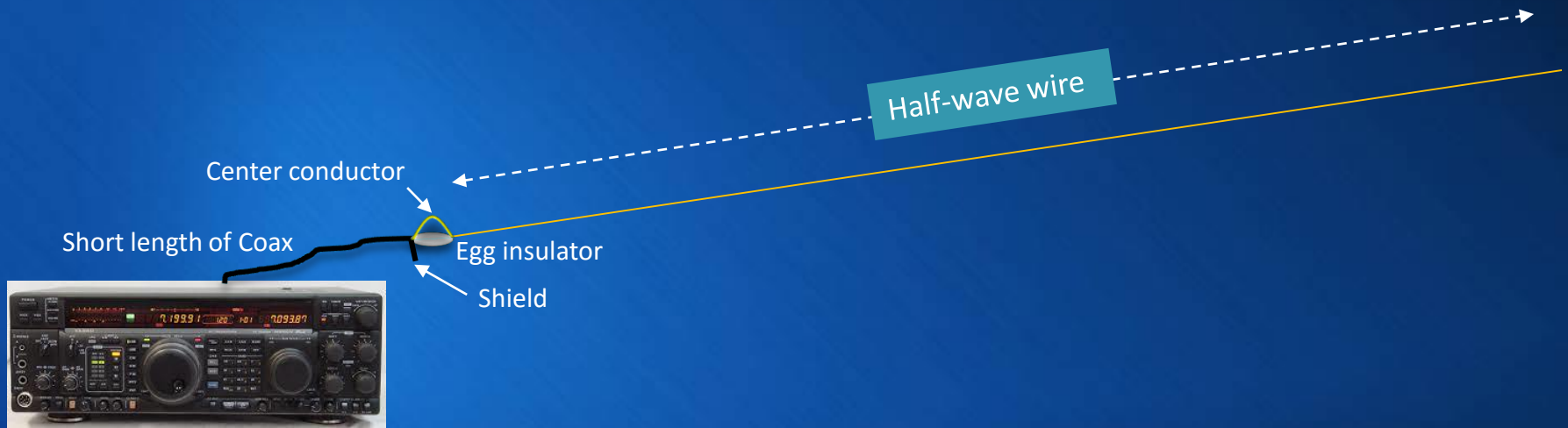- It's very convenient.
- Run the feedline to your window.
- Run a half wave of wire out to a single high point (tree).



Magical

The [^] End-Fed Half Wave Antenna


Rogue Valley Amateur Radio Club

Tom McDermott, N5EG

October 6, 2016


Diagram

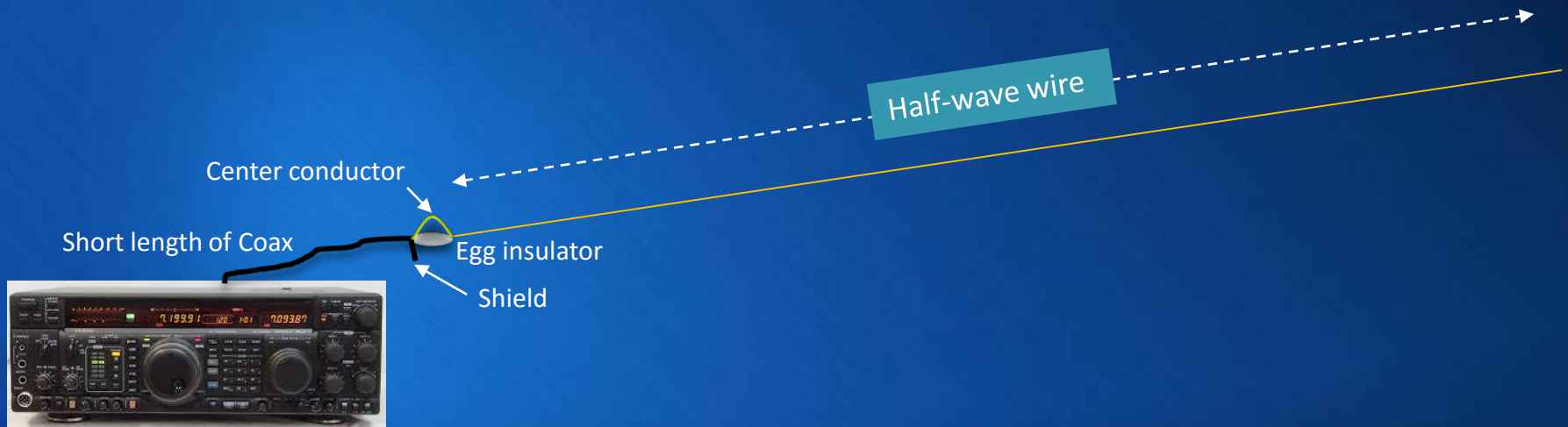- It's very convenient.
- Run the feedline to your window.
- Run a half wave of wire out to a single high point (tree).



- Weird stuff happens...
 - Terrible RFI, RF feedback into my MIC.
 - RF burns when I touch the radio chassis.
 - SWR changes as I move my hands.
 - What the heck is going on ?

Circuit Diagram

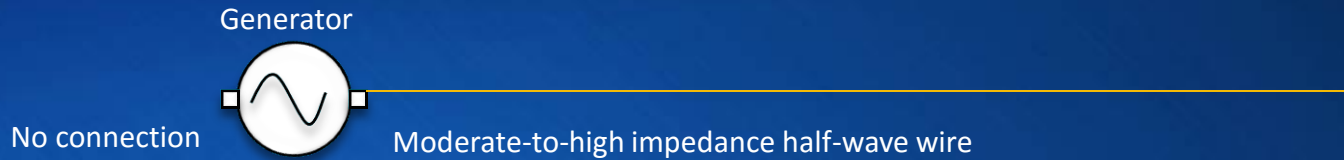

- Kirchhoff's current rule:
 - The sum of currents into a node is zero.
(As much current flows into a node as flows out).
- How much current flows into 'no connection'?
- How much current does the generator supply?
- What's the SWR seen by the generator?
- Does it defy the laws of physics?

Mystical


The Δ End-Fed Half Wave Antenna

Rogue Valley Amateur Radio Club

Tom McDermott, N5EG

October 6, 2016

Circuit Diagram

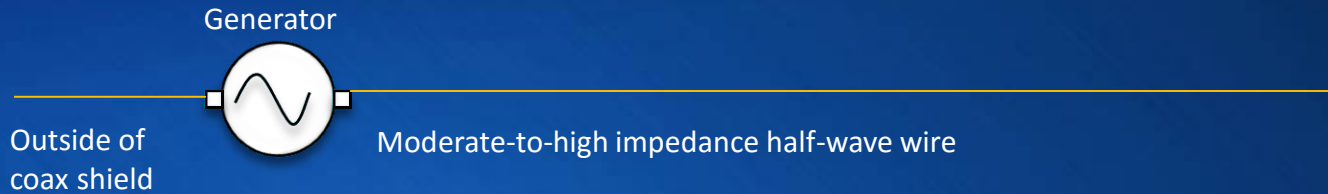

- It's impossible to completely isolate one generator terminal.
 - Direct Cable feed:
 - The outside of the coaxial cable shield is tied to the generator terminal.
 - Completely different currents flow on the outside vs. the inside of the shield !!
 - Balun feed:
 - No balun has perfect isolation.
 - Any real balun has losses.

Mythical


The Δ End-Fed Half Wave Antenna

Rogue Valley Amateur Radio Club

Tom McDermott, N5EG


October 6, 2016

Cable Feed

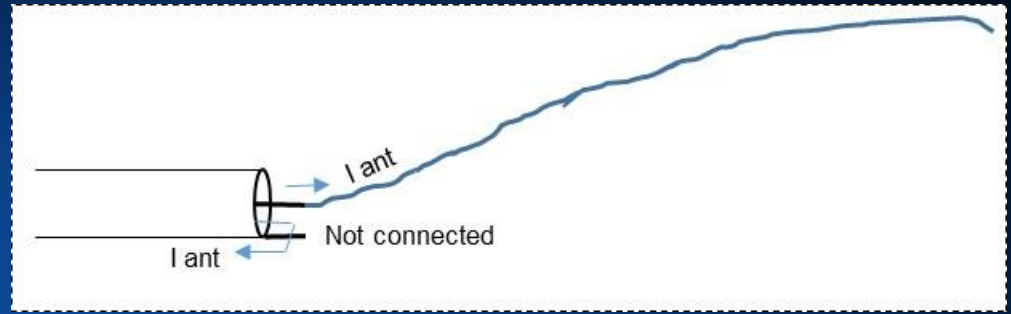

- The cable inside shield current returns back on the cable shield outside.
 - The cable shield forms the 'other half' of the antenna.
 - The antenna is actually off-center fed.
 - The shield (hot part of antenna) is probably wired to the transmitter chassis.
 - Tx is 'hot' with RF (ouch).
 - Touching the transmitter changes the antenna capacitance – the SWR changes as you move around.
 - RFI everywhere !!


Balun Feed

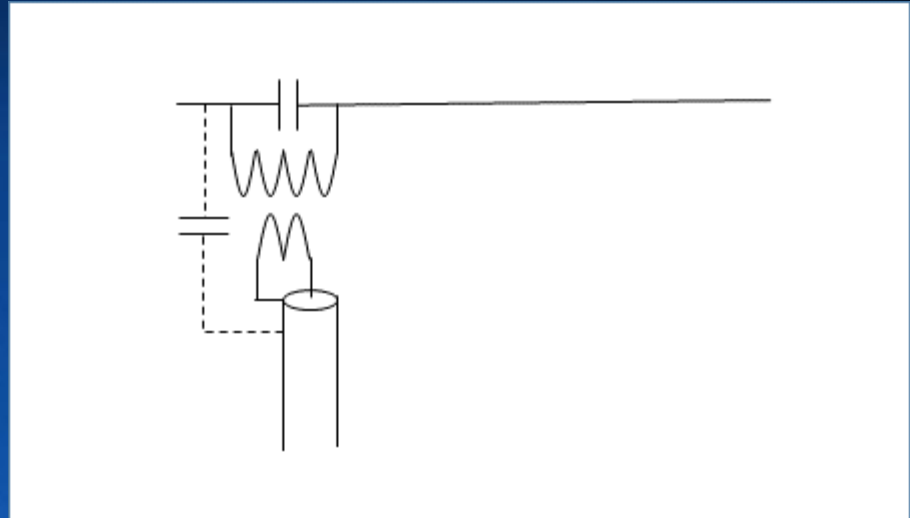

- Current must flow through the balun stray C.
 - If the balun Z is high, then large voltages can appear across the balun. Arc arc...
 - If the balun is lossy, then it can dissipate a lot of power. Ferrite dust...
- At 100 watts the voltage can be thousands of volts RF.
 - Using QRP you may never notice.

Stub Feed

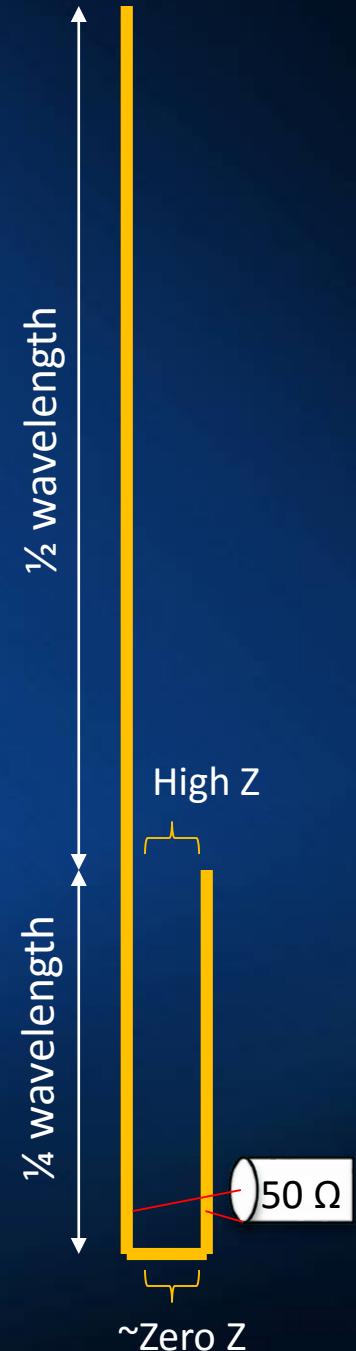- Use a $\frac{1}{4}$ wave stub to transform High-Z to Low-Z.
 - Commonly called “J-pole” antenna
- Stub does not solve common mode problem.
 - No current into top of short stub leg.
 - Current into stub legs must be equal and opposite or else the stub radiates.
 - Feedline shield still radiates.
 - Antenna pattern is strongly dependent on feedline, and placement.



Quarter Wave Wires

- A $\frac{1}{4}$ wave (or $\frac{3}{4}$, $\frac{5}{4}$, etc.) wire is an impedance inverter.
 - If it is 'open' at the far end, the impedance is low at the near end.
 - Current wants to flow into a low impedance.
 - If it is 'shorted' at the far end, the impedance is high at the near end.
- Above applies when in free space.
 - When buried in the ground, its effective length changes a lot.
- It is only a quarter-wave on one band.
- Counterpoise can be in the same plane as the antenna (i.e. dipole).

How to make EFHW work?

- How could we make an EFHW antenna work?
 - Need a finite impedance at both generator terminals.
 - A short connection to good ground is one way.
 - A $\frac{1}{4}$ wave wire (counterpoise) is another way.
 - A grounded $\frac{1}{4}$ wave wire is not a good way.
 - If the antenna is $\frac{1}{2}$ wave, the feed will be unbalanced unless the counterpoise is also $\frac{1}{2}$ wave.
 - A balun could deal with this provided the impedance is reasonable.

